
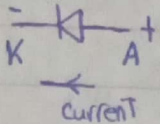


* (Diodes)  (Electronic element Permit current only to Flow in one direction only)


→ Connecting diodes

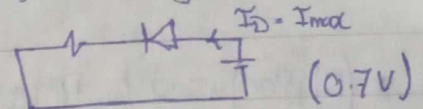(1) Forward Bias: Connecting Positive Pole of the diode with (+ve) of battery and the (-ve) Pole of diode with (-ve) of battery



* Act as Closed Switch


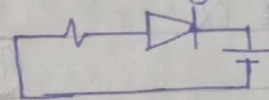
(2) Reverse Bias: Connecting Positive Pole of diode with (-ve) Pole of battery and (+ve) Pole of battery with (-ve) Pole of diode



* Act as opened switch

Rectification: circuit of converting AC current to DC current.

(1)

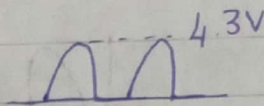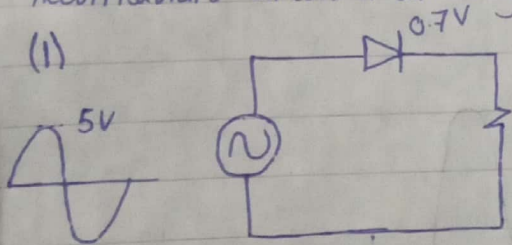


(HALF wave Rectification)

$$V_{dc} = \frac{V_{max}}{\pi} = 0.318 V_{max}$$

* To increase the efficiency of output, capacitor is used

(2)

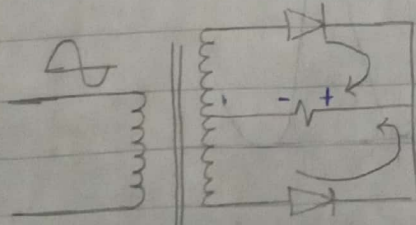

(Full wave Rectification


using 2 diodes)

$$V_{dc} = \frac{2V_{max}}{\pi} = 0.637 V_{max}$$

* its efficiency can be increased by using capacitor

* disadvantage: it needs a "center tapped" (E)


(3)

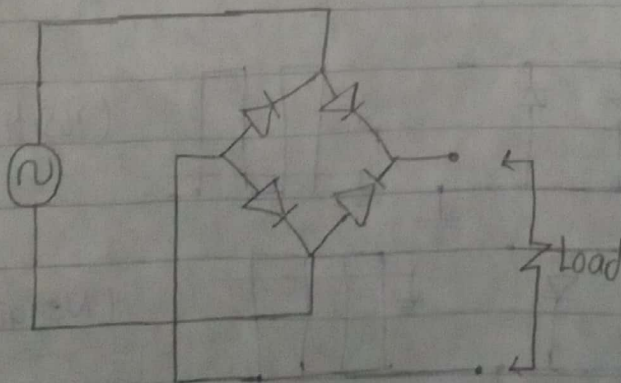

(Full wave Rectification using bridge)

* Capacitor increases efficiency

* Can be Replaced by "Bridge Rectifier"

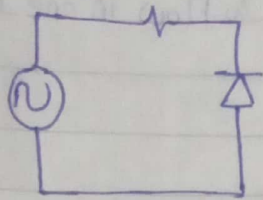


Forward Bias $V = 0.7V$
Reverse " $V = \text{source}$


the diode is on when volt on anode is more than Cathode by $0.7V$

* (clipper) used to protect some devices from a specific volt. (High volt)



EX

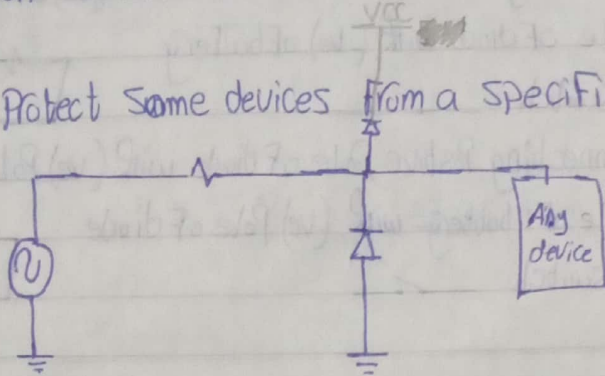


* clamper circuit

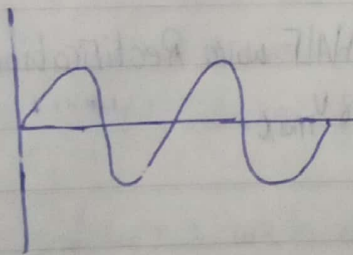

Positive clamper


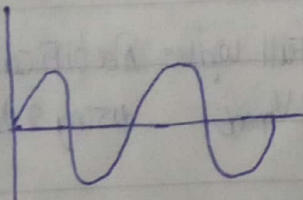
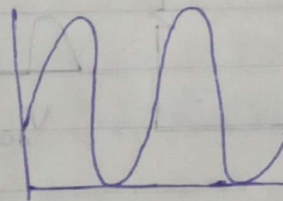


Negative clamper



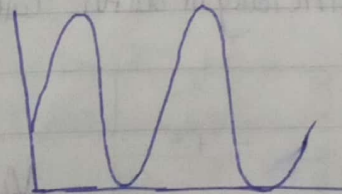


* Function: it is a circuit that works to add a dc voltage on AC current.

* Also it is called "DC Restoration"

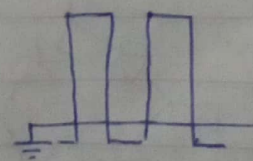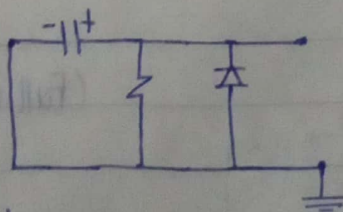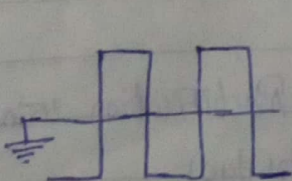


(Positive clamper)

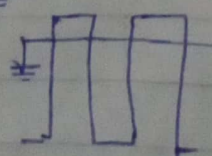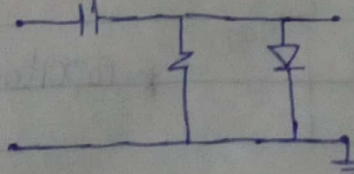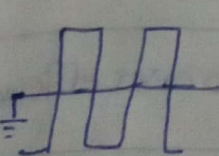

(Negative clamper)

* we can shift the signal more by using battery before diode

Voltage multiplier

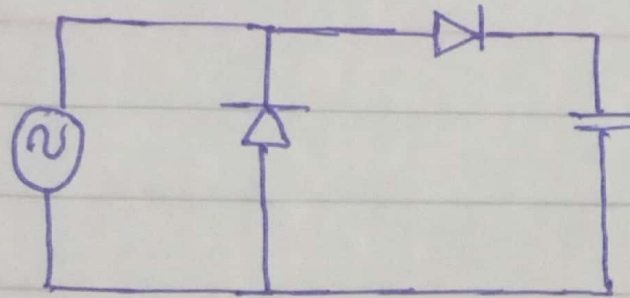

Multiplier = clamper + Rectifier.

→ used to Multiple the input Voltage but the input must be (AC Voltage).